

# **Virginia Tech Training**

**Name: Kholoud Ebrahim Ali Darwesh**

## 1. Write a behavioral model of a single bit full adder.

```
1 module Full_Adder_1_bit (A, B, Cin, Sum, Cout);
2 input A, B, Cin;
3 output reg Sum, Cout;
4 // behavioral model of a single bit full adder
5 always @(*) begin
6     Sum = A ^ B ^ Cin;
7     Cout =(A & B) | (B & Cin) | (A & Cin);
8 end
9 endmodule
```


```
1 `timescale 100ps/1ps
2 module Test_Full_Adder_1_bit ;
3 reg A, B, Cin;
4 wire Sum, Cout;
5 // Testing of behavioral model of a single bit full adder
6 Full_Adder_1_bit DUT1(A, B, Cin, Sum, Cout);
7
8 initial begin
9     Cin=1'b0;
10    A = 1'b0;
11    B = 1'b0;
12    #1
13    B = 1'b1;
14    #1
15    A = 1'b1;
16    #1
17    B = 1'b0;
18    #1
19    A = 1'b0;
20    // it takes only 500ps in simulation
21 end
22
23 initial begin
24     $monitor ("time:%2d    A: %b    B:%b    Sum: %b    Cout: %b\n",
25             $time, A, B, Sum, Cout);
26 end
27 endmodule
```

## The simulation of the first module

	Msgs	
/Test_Full_Adder_1_bit/A	0	
/Test_Full_Adder_1_bit/B	0	
/Test_Full_Adder_1_bit/Cin	0	
/Test_Full_Adder_1_bit/Sum	St0	
/Test_Full_Adder_1_bit/Cout	St0	

```
# time: 0   A: 0   B:0   Sum: 0   Cout: 0
#
# time: 1   A: 0   B:1   Sum: 1   Cout: 0
#
# time: 2   A: 1   B:1   Sum: 0   Cout: 1
#
# time: 3   A: 1   B:0   Sum: 1   Cout: 0
#
# time: 4   A: 0   B:0   Sum: 0   Cout: 0
#
```

## The RTL of the first module

 

## 2. Write a structural model of P-bit full adder.

```
1 module Full_Adder_P_bit #(parameter P=4) (A, B, Cin, Sum, Cout);
2 input Cin;
3 input [P-1:0]A, B;
4 output [P-1:0]Sum;
5 output Cout;
6 wire [P:0]C_internal;
7 // Structural model of P-bit full adder
8 genvar i;
9 generate
10 for (i=0; i< P ; i = i+1) begin : generate_P_bit_FA
11 Full_Adder_1_bit DUT0(.A(A[i]), .B(B[i]), .Cin(C_internal[i]),
12 .Sum(Sum[i]), .Cout(C_internal[i+1]));
13 end
14 endgenerate
15
16 assign C_internal[0] = Cin;
17 assign Cout = C_internal[P];
18 endmodule
```

```
1 `timescale 100ps/1ps
2 module Test_Full_Adder_P_bit;
3 reg Cin;
4 parameter P = 4;
5 reg [P-1:0]A, B;
6 wire [P-1:0]Sum;
7 wire Cout;
8 // Testing of Structural model of P-bit full adder
9 Full_Adder_P_bit #(P(P)) DUT(A, B, Cin, Sum, Cout);
10
11 initial begin
12     Cin= 0;
13     A= 3; B= 1;
14     #1
15     A= 1; B= 2;
16     #1
17     A= 3; B= 3;
18     #1
19     A= 2; B= 1;
20     #1
21     A= 0; B= 3;
22 end
23
24 initial begin
25 $monitor ("time: %2d    A: %b    B: %b    Sum: %b    Cout: %b",
26 $time, A, B, Sum, Cout);
27 end
28 endmodule
```


## The simulation of the second module

[illegible]

```
VSIM 8> run
```

```
# time: 0   A: 0011   B: 0001   Sum: 0100   Cout: 0
# time: 1   A: 0001   B: 0010   Sum: 0011   Cout: 0
# time: 2   A: 0011   B: 0011   Sum: 0110   Cout: 0
# time: 3   A: 0010   B: 0001   Sum: 0011   Cout: 0
# time: 4   A: 0000   B: 0011   Sum: 0011   Cout: 0
```

### The RTL of the second module

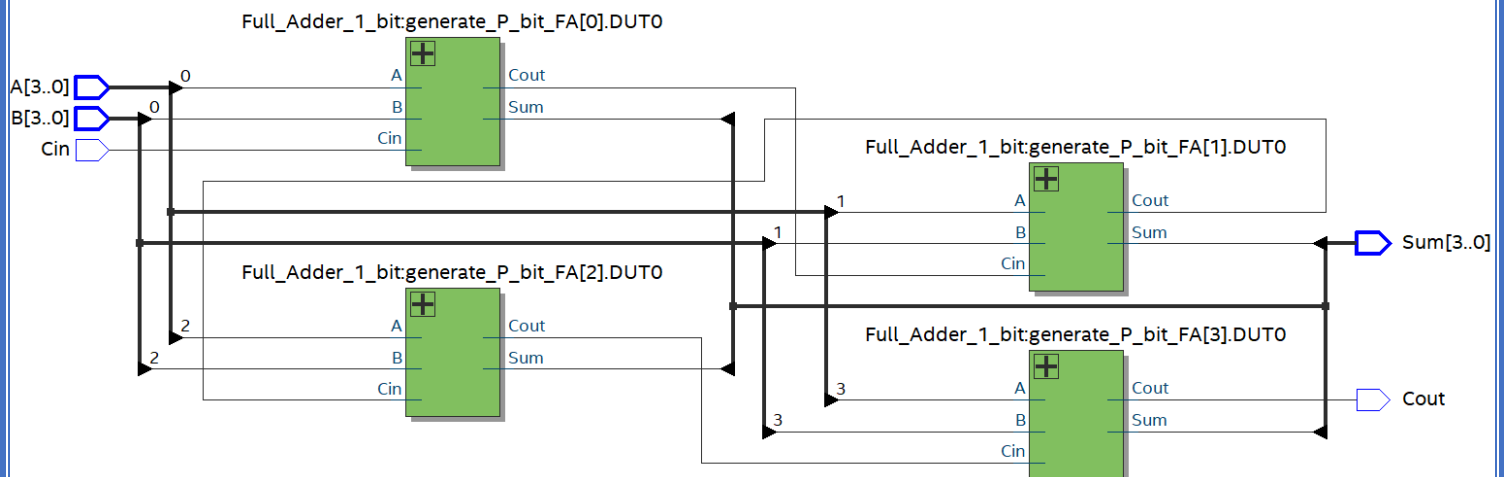

### 3. Write a behavioral model of M-bit by N-bit Multiplier.

```
1  module Multiplier_M_N_bits #(parameter M=4, N=3) (num1, num2, Result);
2  input  [M-1:0]num1;
3  input  [N-1:0]num2;
4  output reg [M+N-1:0]Result;
5  reg    [M+N-1:0]Mul_stage;
6  reg    [M+N-1:0]Mul_Register[N-1:0];
7  integer i;
8  // behavioral model of M-bit by N-bit Multiplier
9  always @(*) begin
10     Result = 0;
11     for (i=0; i< N ; i = i+1) begin :Multiplier_Register
12         Mul_stage = num1 & {M{num2[i]}};
13         Mul_stage = Mul_stage << i;
14         Mul_Register[i]= Mul_stage;
15         Result= Mul_Register[i]+Result;
16     end
17 end
18 endmodule
```


```
1  `timescale 100ps/1ps
2  module Test_Multiplier_M_N_bits;
3  parameter M= 6,N= 4;
4  reg    [M-1:0]num1;
5  reg    [N-1:0]num2;
6  wire  [M+N-1:0]Result;
7
8  Multiplier_M_N_bits #(M(M), .N(N)) DUT(num1, num2, Result);
9
10 initial begin
11     num1 = 63; num2 = 15;
12     #1
13     num1 = 0; num2 = 3;
14     #1
15     num1 = 27; num2 = 9;
16     #1
17     num1 = 12; num2 = 31;
18     #1
19     num1 = 20; num2 = 0;
20     #1
21     num1 = 32; num2 = 7;
22 end
23
24 initial begin
25     $monitor("time: %2d    num1: (%d)%b    num2: (%d)%b    Result: (%d)%b",
26             $time, num1, num1, num2, num2, Result, Result );
27 end
28 endmodule
```

## The simulation of the third module


	Msgs	
/Test_Multiplier_M_N_bits/M	6	6
/Test_Multiplier_M_N_bits/N	4	4
/Test_Multiplier_M_N_bits/num1	100000	111111 000000 011011 001100 010100
/Test_Multiplier_M_N_bits/num2	0111	1111 0011 1001 1111 0000
/Test_Multiplier_M_N_bits/Result	0011100000	1110110001 0000000000 0011110011 0010110100 0000000000

```
# time: 0  num1: (63)111111  num2: (15)1111  Result: ( 945)1110110001
# time: 1  num1: ( 0)000000  num2: ( 3)0011  Result: (  0)0000000000
# time: 2  num1: (27)011011  num2: ( 9)1001  Result: (243)0011110011
# time: 3  num1: (12)001100  num2: (15)1111  Result: (180)0010110100
# time: 4  num1: (20)010100  num2: ( 0)0000  Result: (  0)0000000000
```

## The RTL of the third module

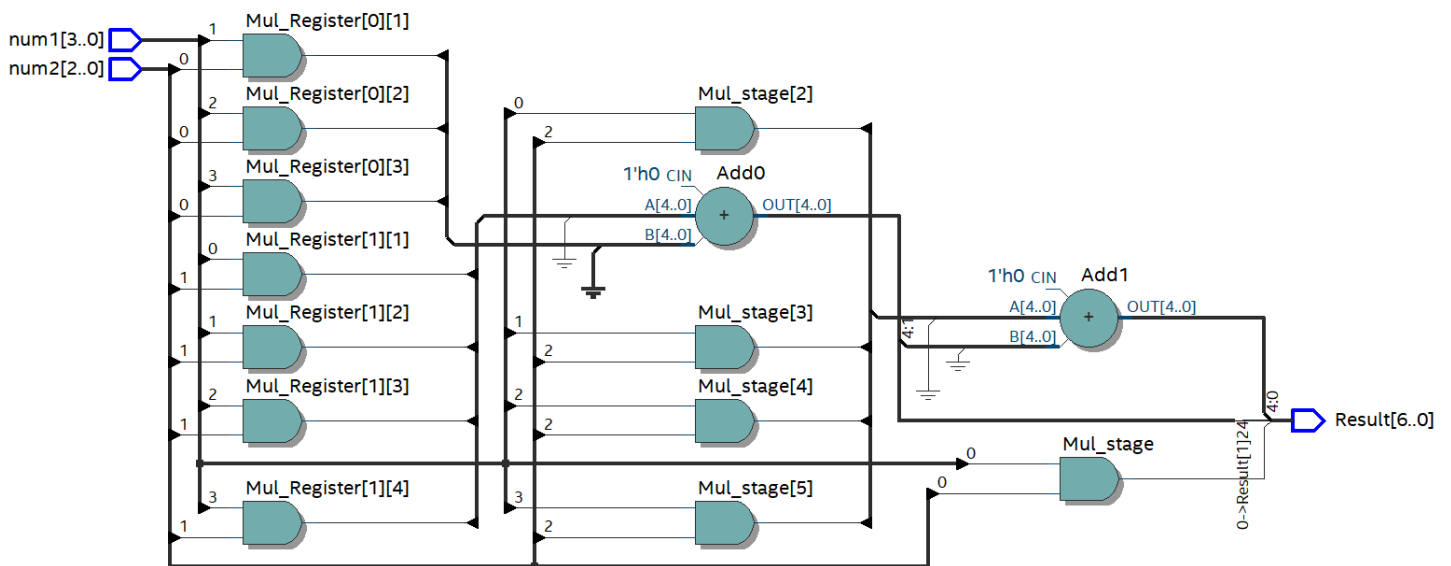
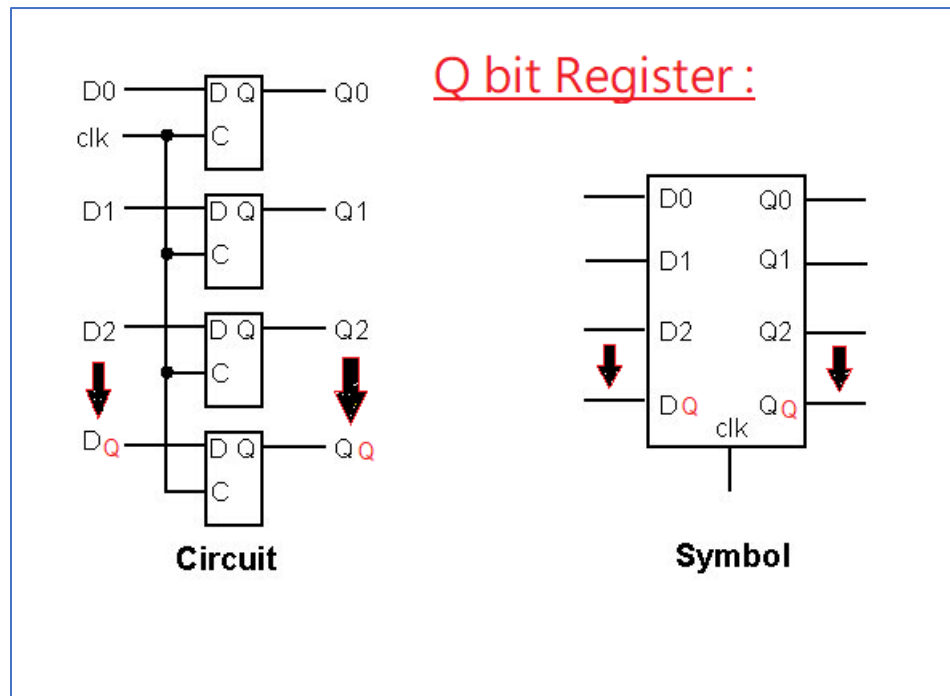
#### 4. Write a behavioral model of a Q-bit Register.



```
1  module Register_Q_bit #(parameter Q = 4) (clk, rst, in, out);
2  input  [Q-1:0] in;
3  input  clk, rst;
4  output reg [Q-1:0] out;
5
6  // behavioral model of a Q bit Register
7  always @(posedge clk, posedge rst)
8  begin
9      if (rst)
10         out <= 0;
11     else
12         out <= in;
13 end
14 endmodule
```



```

1  `timescale 1ps/1ps
2  module Test_Register_Q_bit;
3  parameter Q= 3;
4  reg  [Q-1:0]in;
5  reg  clk, rst;
6  wire [Q-1:0]out;
7
8
9  Register_Q_bit #(Q)RG(clk, rst, in, out);
10
11  initial begin
12      clk =1;
13      forever #50  clk =~clk;
14  end
15
16  initial begin
17      rst =1;
18      #100  rst =0; // rst in one clock cycle
19  end
20
21  initial begin
22      // the change in input will be at the negative edge ,
23      //which can be detected at the next posetve edge of the clock
24      in=2; #150
25      in=1; #100
26      in=6; #100
27      in=7; #100;
28  end
29
30  initial begin
31      $monitor ("time: %3d    in: %b    out: %b ",
32              $time          , in      , out      );
33  end
34  endmodule


```

## The simulation of the fourth module


	Msgs	
/Test_Register_Q_bit/Q	3	3
/Test_Register_Q_bit/in	111	010
/Test_Register_Q_bit/dk	1	001
/Test_Register_Q_bit/rst	0	110
/Test_Register_Q_bit/out	111	111
		000
		010
		001
		110
		111

```
# time: 0   in: 010   out: 000
# time: 100  in: 010   out: 010
# time: 150  in: 001   out: 010
# time: 200  in: 001   out: 001
# time: 250  in: 110   out: 001
# time: 300  in: 110   out: 110
# time: 350  in: 111   out: 110
# time: 400  in: 111   out: 111
```

## The RTL of the fourth module

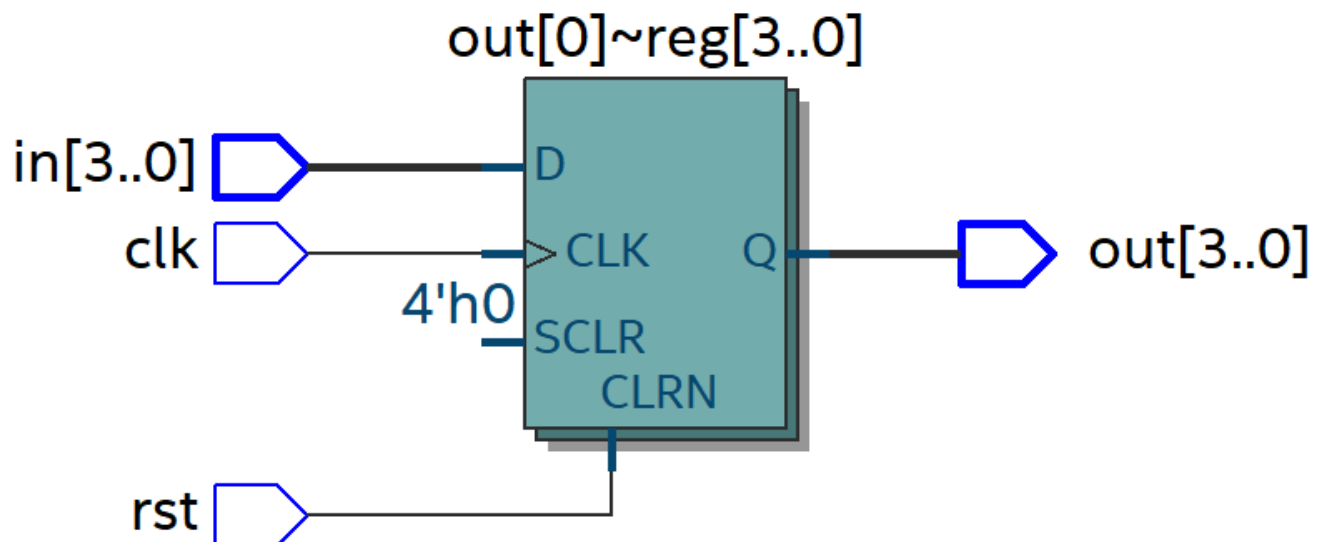
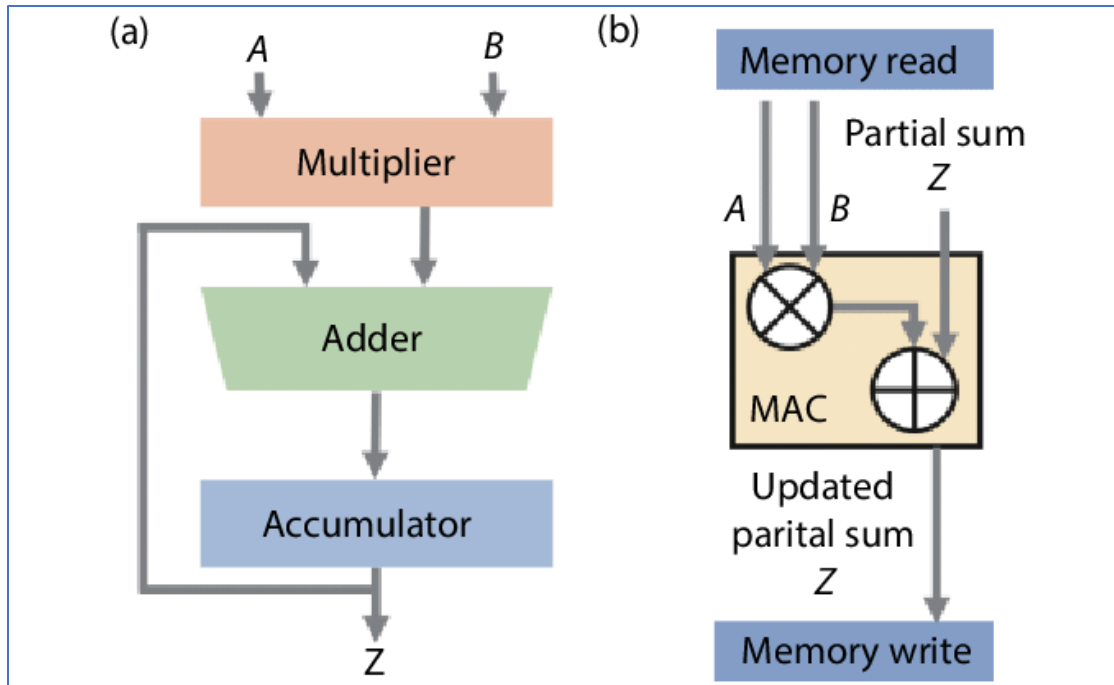
## 5. Write a structural model of a MAC Unit.



```

1  module MAC_Unit#(parameter M=8, N=8, P=16, Q=16) (clk , rst, A, B, Cout, Z);
2
3  input  rst, clk;
4  input  [M-1:0]A;
5  input  [N-1:0]B;
6  output [M+N-1:0]Z;
7  output Cout;
8  wire   [M+N-1:0]Mul;    // the out of multiplication operation
9  wire   [M+N-1:0]add;    // the out of addition
10
11  // Structural model of a MAC Unit
12  Multiplier_M_N_bits #(M,N) Multp (A, B, Mul);
13  Full_Adder_P_bit    #(P)   Adder (Mul, Z, 1'b0, add, Cout);
14  Register_Q_bit      #(Q)   RegBit(clk, rst, add, Z);
15  endmodule

```

```

1  `timescale 1ps/1ps
2  module Test_MAC_Unit;
3  parameter M = 8, N = 8, P = 16, Q = 16;
4  reg  rst, clk;
5  reg  [M-1:0]A;
6  reg  [N-1:0]B;
7  wire [M+N-1:0]Z;
8  wire Cout;
9
10 MAC_Unit#(M, N, P, Q)MAC(clk , rst, A, B, Cout, Z);
11 initial begin
12     clk =1;
13     forever #50  clk =~clk;
14 end
15 initial begin
16     rst =1;
17     #100  rst =0; // rst in one clock cycle
18 end
19 initial begin
20     // the change in input will be at the negative edge ,
21     //which can be detected at the next posetve edge of the clock
22     A=2; B=3; #150
23     A=1; B=2; #100
24     A=6; B=4; #100
25     A=7; B=1; #100;
26 end
27 initial begin
28     $monitor ("time: %3d    A: %b    B: %b    Z: %b ",
29             $time           , A      , B      , Z      );
30 end
31 endmodule

```

## The simulation of the top module

	Msgs	
/Test_MAC_Unit/M	8	8
/Test_MAC_Unit/N	8	8
/Test_MAC_Unit/P	16	16
/Test_MAC_Unit/Q	16	16
/Test_MAC_Unit/rst	0	
/Test_MAC_Unit/dk	1	
/Test_MAC_Unit/A	00000111	00000010 00000001 00000110 00000111
/Test_MAC_Unit/B	00000001	00000011 00000010 00000100 00000001
/Test_MAC_Unit/Z	0000000000101110	0000000000000000 000000000000110 0000000000001000 0000000000100000 0000000000100111
/Test_MAC_Unit/Cout	St0	

```
# time: 0    A: 00000010    B: 00000011    Z: 0000000000000000
# time: 100  A: 00000010    B: 00000011    Z: 00000000000000110
# time: 150  A: 00000001    B: 00000010    Z: 00000000000000110
# time: 200  A: 00000001    B: 00000010    Z: 000000000000001000
# time: 250  A: 00000110    B: 00000100    Z: 000000000000001000
# time: 300  A: 00000110    B: 00000100    Z: 000000000000100000
# time: 350  A: 00000111    B: 00000001    Z: 000000000000100000
# time: 400  A: 00000111    B: 00000001    Z: 000000000000100111
```

## The RTL of the top module

